

CS2100 Computer Organisation
Lab 09: Gate-Level and Block-Level Design (Week 4th November)
Instruction

Short and clean


We have separated the lab information into i) **instruction** and ii) **report**. Whenever there is a question in the instruction (easily identified as they have **[X pts]** tagged to the end), write / type your answer in the corresponding location in the **report** document. Please take note of the submission specification at the end of this document.

Objective

 1. To learn the difference between gate-level design and block-level design.
2. To learn the behavior of parallel adder.

New components in Digital

Fire up **Digital** and use “File→Open” to open the provided “Lab 09 – Circuit Template.dig”. The template circuit contains the inputs, outputs and the two required components for this lab (NAND gate and a 4-bit Cascade Adder / Parallel Adder). There are three new **Digital** components, captured below in one example to illustrate their functionality:



- **[Constant Values]** Provide the constant 0 (false) or 1 (true) for your circuit. Use these if you find that you need to tie the input of a component to a 0 or 1 permanently.
- **[Multi-Bit Value]** The “input” and “output” component can be set to multiple bits. The example here is a 5-bit output. Benefits includes meaningful display of the 5 bits as a single value, e.g. the above show the 5-bit 10010 as 18_{10} .
- **[Splitter-Merger]** This component allows us to merger or split input / output. The example shown above merge 5 1-bit input into a single 5-bit output.

Procedure:

1. You are to design a **multiply-by-6** circuit given a 3-bit binary unsigned value ABC as its input. The circuit generates a 5-bit binary number $S_4 S_3 S_2 S_1 S_0$, and an output V .

Since the circuit may not accommodate certain input value owing to the limited number of output bits, **such an input value is deemed invalid**, and the corresponding output will be **don't-care values**. The output V is used to indicate whether the input value is valid or not: **1** if the input value is valid, or **0** otherwise.

Give the truth table in report. **[4 pts]**

2. **[Gate-Level Design]** Give the K-maps for S_4, S_3, S_2, S_1 and S_0 . Write out the simplified SOP (sum-of-products) expression for each of them. **[5 pts]**

3. **[Block Level Design]** Instead of using the results from (2), let's implement the multiply-by-6 circuit using a 4-bit cascade adder (parallel adder). The 4-bit adder is used to generate the 5-bit output $S_4 S_3 S_2 S_1 S_0$. [Hint: Think in binary ☺]

For the output V , you are to use a NAND gate to implement it.

Design your circuit in **Digital** and paste a screenshot of the complete circuit into the report.

You are not allowed to add any additional digital logic component (i.e. you can solve the lab just by connecting the components). Note that the output " S " is a 5-bit value, connect the $S_4 S_3 S_2 S_1 S_0$ accordingly. You can add more constants (1 / 0) components to reduce wiring mess. **[7 pts]**

4. Implement the circuit in (3). Show your circuit to your lab TA. **[4 pts]**

Common Errors:

- Remember to connect **all** inputs to some values (remember the **constant values**).
- Misread the significance of the multi-bit values. The " 0^{th} index" is the **least significant** bit.

You need to submit into Luminus Folder no longer than **2359 on the same day** you have the online lab. Please rename the **report document** with your student id: **[student_id]_lab08.docx** or **[student_id]_lab08.pdf**, e.g. **A1234567X_lab08.pdf**. Submit into the correct folder on Luminus before 2359 of your lab day.

Marking Scheme: Report – 16 marks; Demonstration – 4 marks; Total: 20 marks.