

## CS2100 Logic Circuit Guidelines

This is a quick guide on the expected standard of all logic circuit drawing in CS2100. Make sure you follow the guideline while giving answers for the lab and final assessment.

- Please write and draw clearly and neatly. You may use pencil for logic diagrams. Untidy writing or drawing will be penalized.
- Please draw large and neat circuit diagrams. See some real students' samples below.

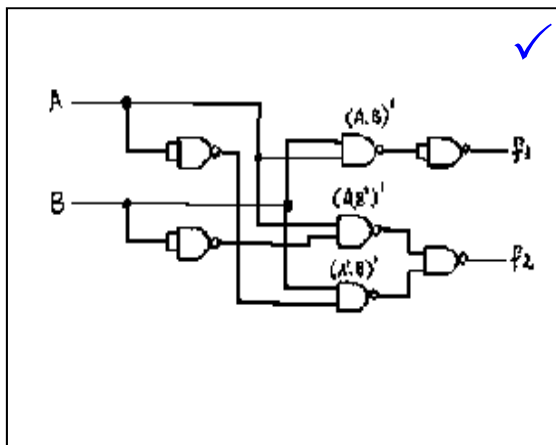


Figure 1. Good example.

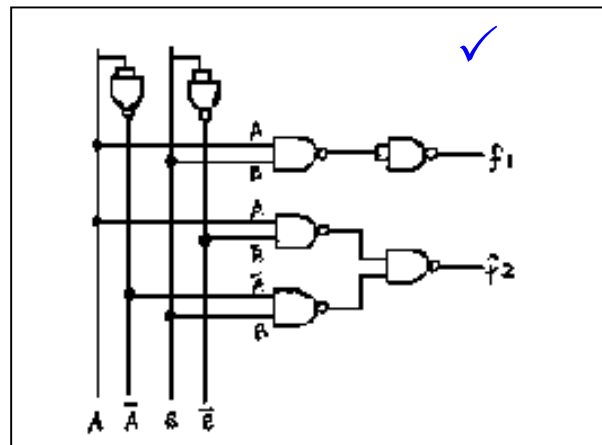


Figure 2. Good example.

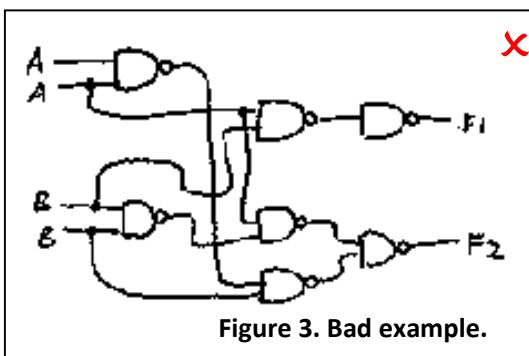


Figure 3. Bad example.


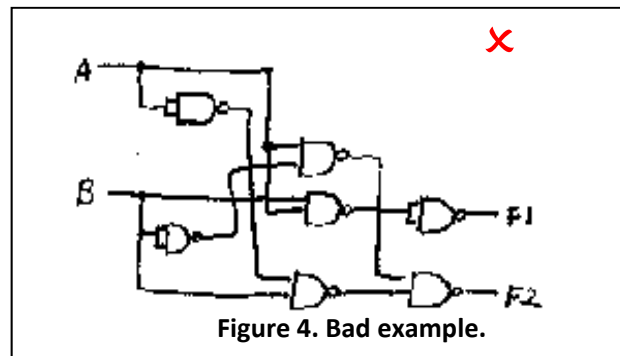



Figure 4. Bad example.

- For logic diagrams, all lines should be straight. All inputs, outputs and intermediate outputs should be labeled, as shown in Figure 5. Use black dot to indicate a fork.

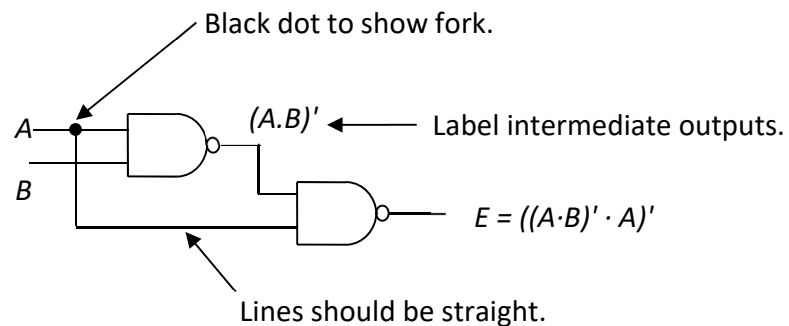


**Figure 5.**

- All inputs of a gate must be fed with some value. You should not leave any input unconnected. For example, to use a 2-input NAND gate as an inverter, here are two correct methods:

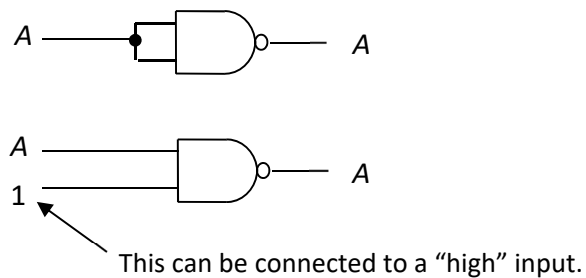

**Figure 6.**

But this is wrong:

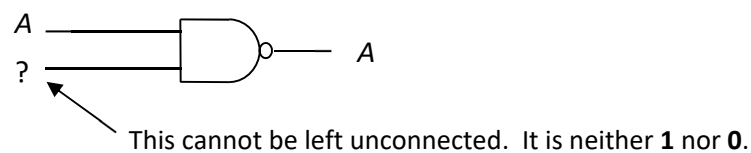

**Figure 7.**

~~~ End of Guide ~~~